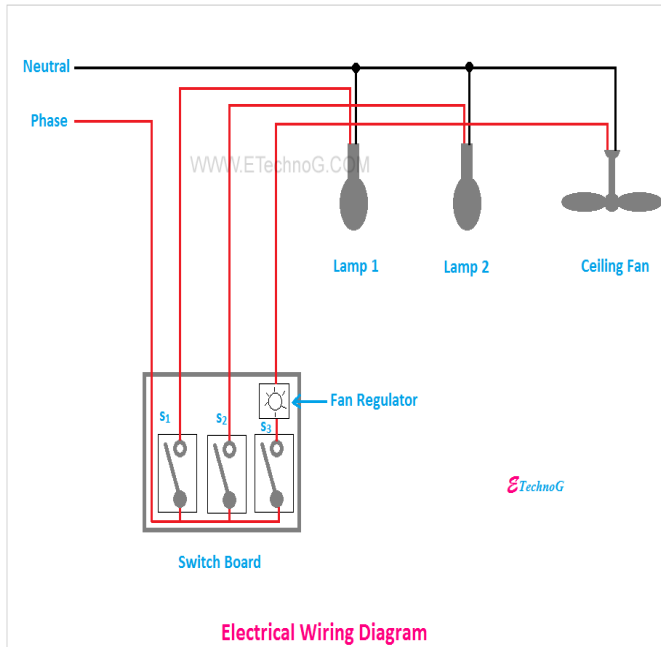



CAED- (Module 5): Multi-disciplinary applications and practice
(CO6)- Rough sketches only - Only for Test-2 not for Final Exam-

Electrical/Electronic wiring diagrams:


Electrical wiring for Lighting:



Electrical wiring for calling bell:

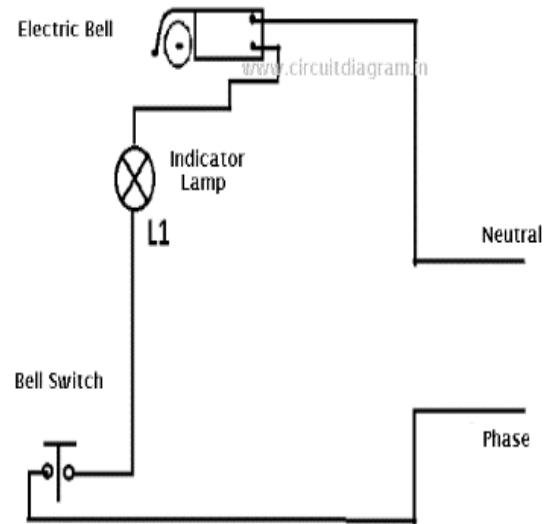

Electronic circuit:

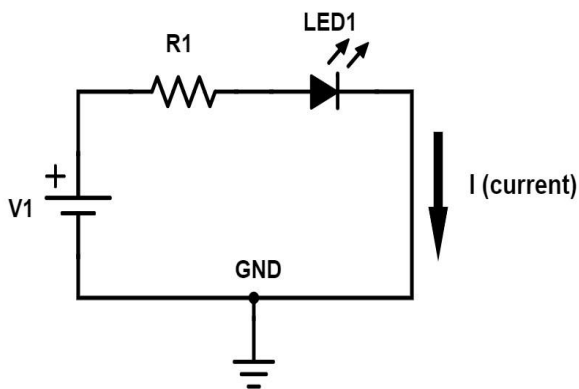

DC Motor circuit:

